



# Intel Memory Architecture



## Topic # 8

Fall 2020



# Book Reference

- Intel Microprocessor by Barry B. Brey  
(8<sup>th</sup> Edition)
- Chapter 10





# Basics of Memory Architecture

## ➤ Stores large number of bits

- $m \times n$ :  $m$  rows of  $n$  bits each
- $k = \text{Log}_2(m)$  address input signals
- or  $m = 2^k$  rows
- e.g., 4k x 8 memory:  
12 address inputs  
8 data lines
  
## ➤ Memory access

- **r/w**: selects read or write
- **enable**: read or write only when asserted





# Memory Types

## ➤ Traditional ROM/RAM distinctions

- **ROM**

read only, bits stored without power

- **RAM**

read and write, lose stored bits without power

## ➤ Traditional distinctions blurred

- Advanced ROMs can be written to

e.g., **EEPROM**

- Advanced RAMs can hold bits without power

e.g., **NVRAM, DDRAM**

## ➤ Write Ability

- Speed, a memory can be written

## ➤ Storage Permanence (Reliability)

- ability of memory to hold stored bits after they are written



# Write Ability

## ➤ Ranges of Write Ability

- **High End**  
processor writes to memory simply and quickly  
e.g., RAM
- **Middle Range**  
processor writes to memory, but slower  
e.g., FLASH, EEPROM
- **Lower Range**  
special equipment, “programmer”, must be used to write to memory  
e.g., EPROM, OTP ROM
- **Low End**  
bits stored only during fabrication  
e.g., Mask-programmed ROM



# Performance (Reliability)

## ➤ Range of Storage Permanence

- **High End**

essentially never loses bits  
e.g., mask-programmed ROM

- **Middle Range**

holds bits days, months, or years after memory's power source turned off  
e.g., NVRAM

- **Lower Range**


holds bits as long as power supplied to memory  
e.g., SRAM

- **Low End**

begins to lose bits almost immediately after written  
e.g., DRAM



# Performance

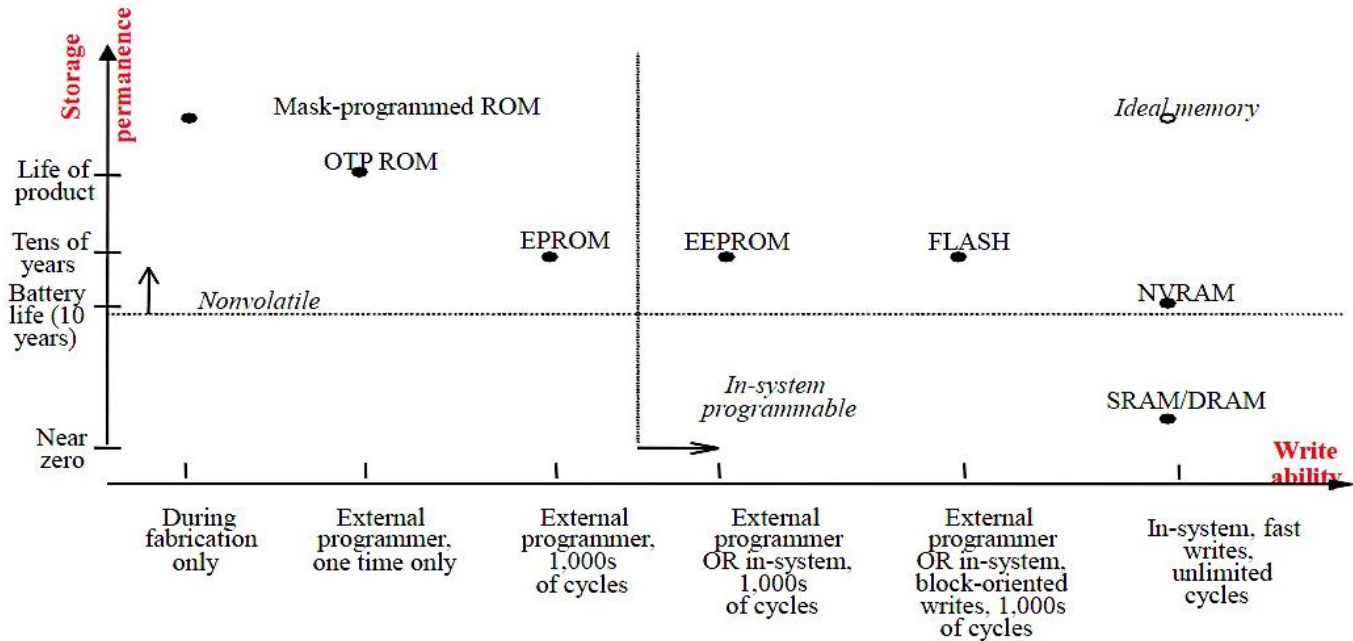

Write ability and storage permanence of memories, showing relative degrees along each axis (not to scale).




# Basic Types of RAM

## ➤ SRAM: Static RAM

- Memory cell uses Flip-Flop to store a Bit
- Requires 6 Transistors
- Holds Data as long as power supplied

### Memory Cell Internals

 






# Basic Types of RAM

## ➤ SRAM: Static RAM

- Memory cell uses Flip-Flop to store a Bit
- Requires 6 Transistors
- Holds Data as long as power supplied

SRAM

### Memory Cell Internals

 




# Basic Types of RAM

## ➤ SRAM: Static RAM


- Memory cell uses Flip-Flop to store a Bit
- Requires 6 Transistors
- Holds Data as long as power supplied

### Memory Cell Internals

 

 
## ➤ DRAM: Dynamic RAM

- Memory cell uses MOS transistor and capacitor to store a bit
- More compact than SRAM
- “Refresh” required due to capacitor leakage
- word's cells refreshed when read
- Typical refresh rate 15.625 micro sec
- **Slower to access than SRAM**



# Composing Memory

 




# Composing Memory

- **Memory Size needed often differs from size of readily available Memories**
  - Required size **4K x 16** but available size is **2K x 8**
- When **available Memory is larger**
  - simply ignore unneeded high-order address bits and higher data lines
- When **available Memory is smaller**
  - compose several smaller memories into one larger memory


 
# Composing Memory


- Connect side-by-side to increase width of words




 
# Composing Memory


- Connect side-by-side to increase width of words




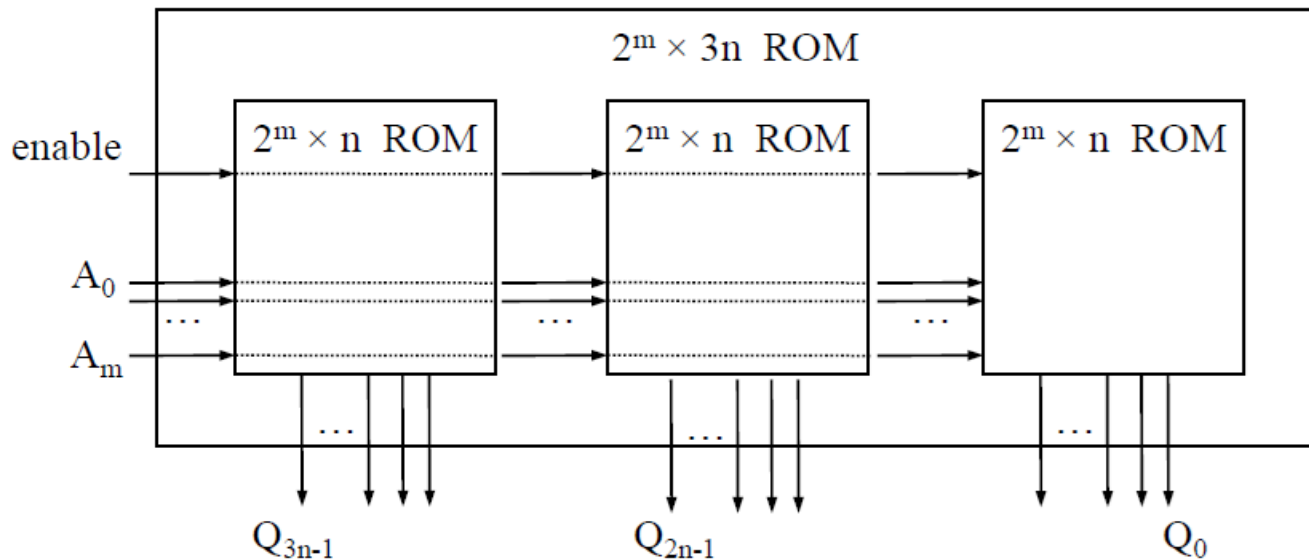
# Composing Memory


- Connect side-by-side to increase width of words




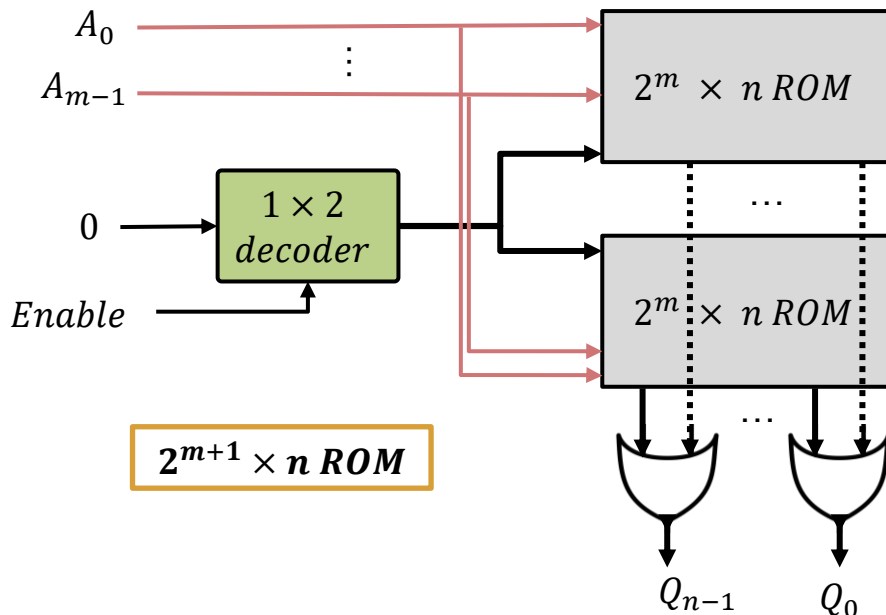
# Composing Memory

- Connect **top to bottom** to increase number of words
  - Added high-order address line selects smaller memory containing desired word using a decoder







 
# Composing Memory: Decoder


- Connect **top to bottom** to increase number of **words**
  - Added high-order address line selects smaller memory containing desired word using a decoder




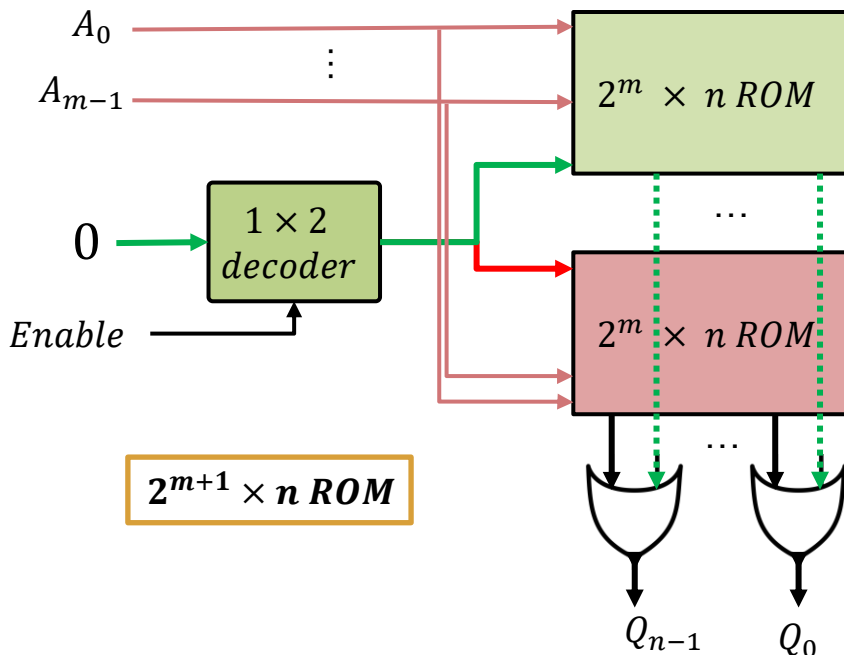
# Composing Memory


- Connect **top to bottom** to increase number of words
- Added high-order address line selects smaller memory containing desired word using a decoder




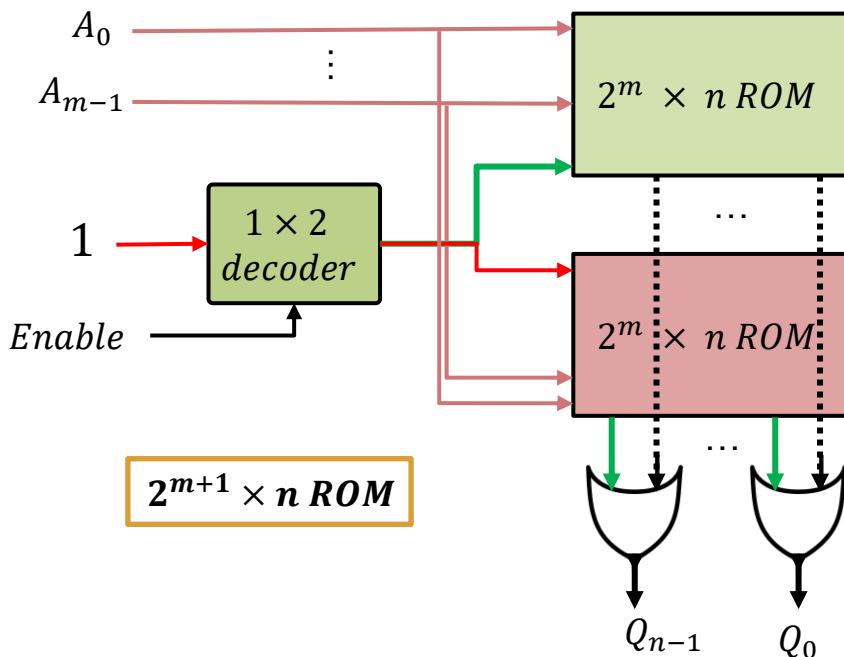
# Composing Memory


- Connect **top to bottom** to increase number of words
- Added high-order address line selects smaller memory containing desired word using a decoder




 
# Composing Memory

- **Combine techniques** to increase number and width of words





# Activity


➤ Compose 1K x 8 ROM  
into a 2K x 16 ROM





# Activity

- Compose 1K x 8 ROM into a 2K x 16 ROM

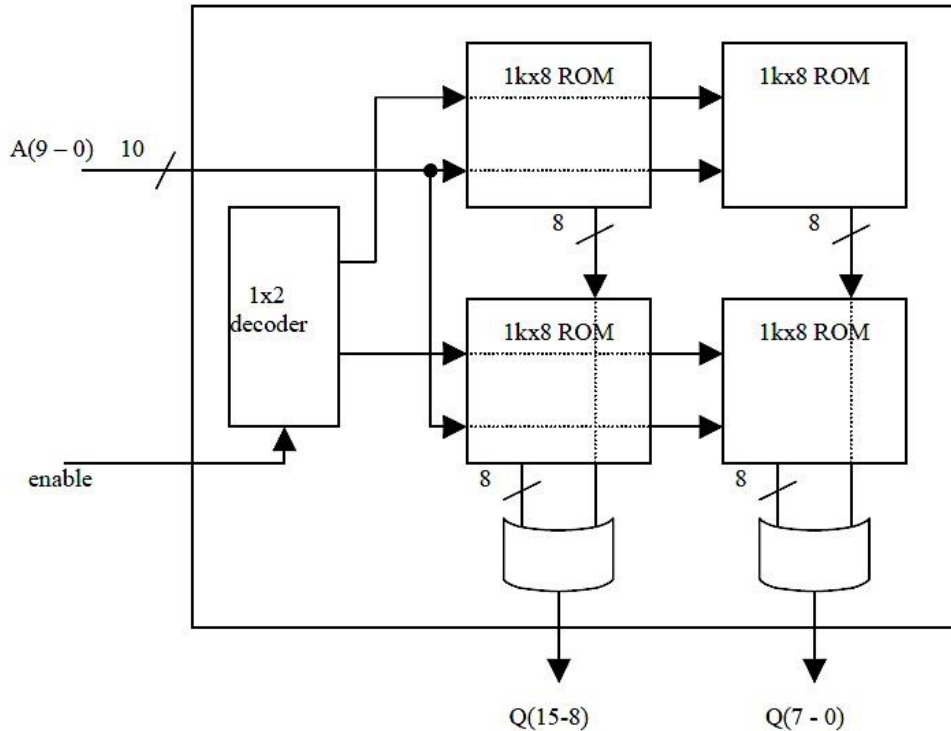




# Interfacing Signals

## ➤ Interfacing memory with CPU


- Address Lines
- Data Lines
- Control Lines

Enable, Read, Write, Ready, Size etc.

 



# 8088 Minimum Memory Interface

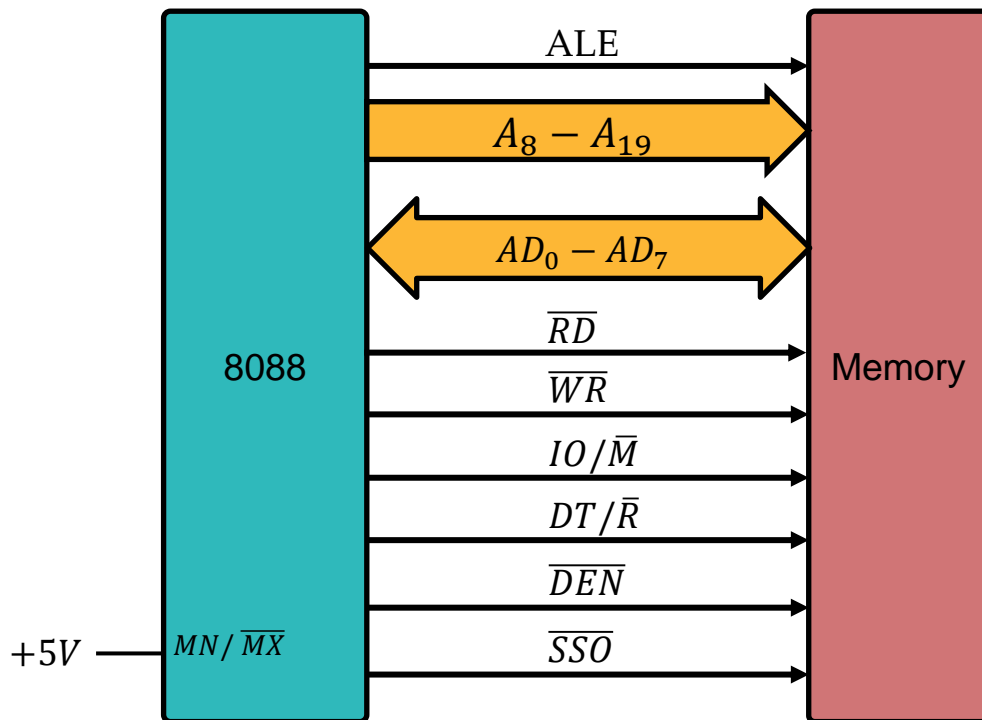

Minimum-mode 8088 memory interface





# Memory Control Signals

$ALE$

**Address Latch Enable** : used to latch the address in external memory

$IO/\bar{M}$

**Input-output/Memory** : signal external circuitry whether memory or I/O bus cycle in progress

$DT/\bar{R}$

**Data Transmit/Receive** : signal external circuitry whether 8088 is transmitting or receiving data over the bus.

$\overline{WR}$

**Write** : identifies a write cycle in progress

$\overline{RD}$


**Read** : identifies a read cycle in progress

$\overline{DEN}$

**Data Enable** : used to enable data bus.

$\overline{SSO}$

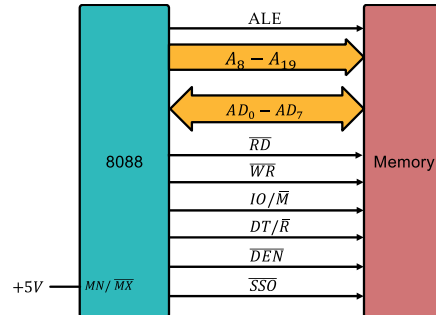
**Status Line** : identifies whether a code or data access is in progress



Minimum-mode 8088 memory interface



# 8088 : Maximum Memory Interface

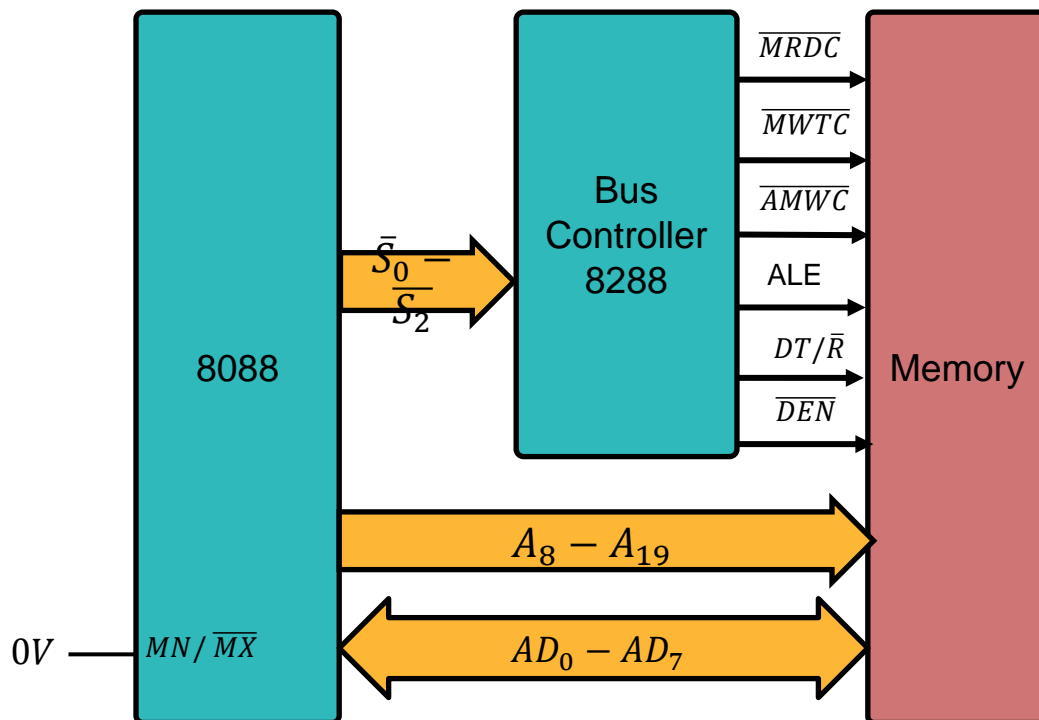

**Maximum-mode 8088 memory interface**




# Memory Control Signals

- Maximum Mode Memory Control Signals

$\overline{MRDC}$  – Memory Read Command

$\overline{MWTC}$  – Memory Write Command

 $\overline{AMWC}$  – Advanced Memory Write Command




Maximum-mode 8088 memory interface

Status Inputs			CPU Cycle	8288 Command
$\overline{S_2}$	$\overline{S_1}$	$\overline{S_0}$		
0	0	0	Interrupt Acknowledge	$\overline{INTA}$
0	0	1	Read I/O Port	$\overline{IORC}$
0	1	0	Write I/O Port	$\overline{IOWC}, \overline{AIOWC}$
0	1	1	Halt	None
1	0	0	Instruction Fetch	$\overline{MRDC}$
1	0	1	Read Memory	$\overline{MRDC}$
1	1	0	Write Memory	$\overline{MWTC}, \overline{AMWC}$
1	1	1	Passive	None




# 8088 Memory Read Cycle (min. mode)

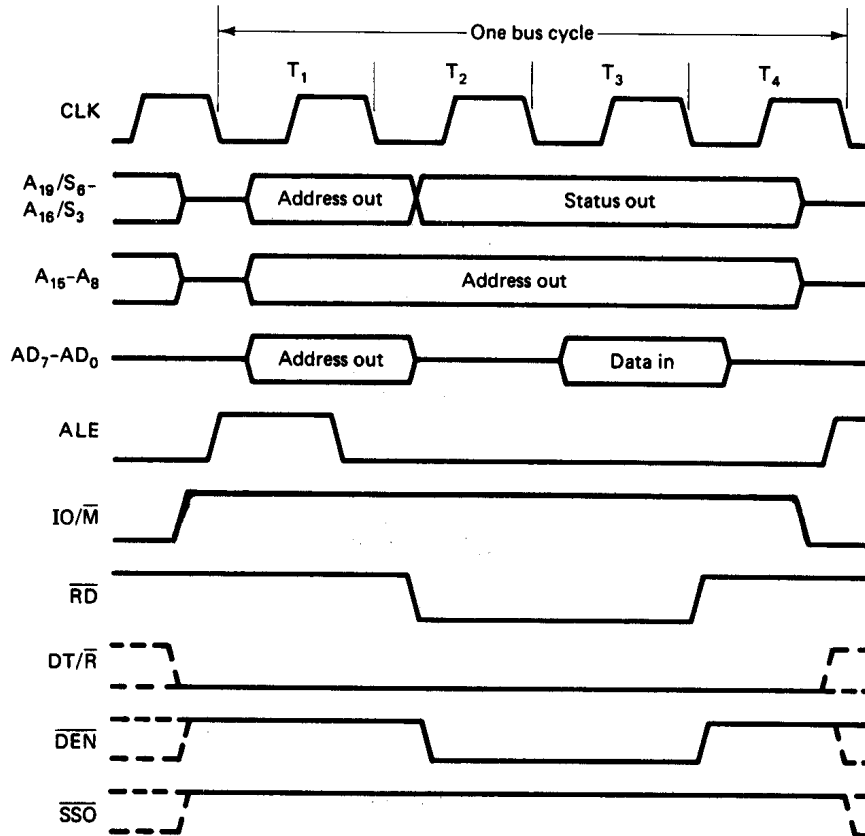



# 8088 Memory Write Cycle (min. mode)

 




# Reading Assignment




- Maximum Mode Read and Write Memory Bus cycles




# Hardware Organization

 

D7-D0  
8088 microprocessor

 

D15-D8

 


D7-D0

8086 microprocessor (memory is only 1M bytes)  
80286 microprocessor  
80386SX microprocessor  
80386SL microprocessor (memory is 32M bytes)  
80386SLC microprocessor (memory is 32M bytes)



# Hardware Organization

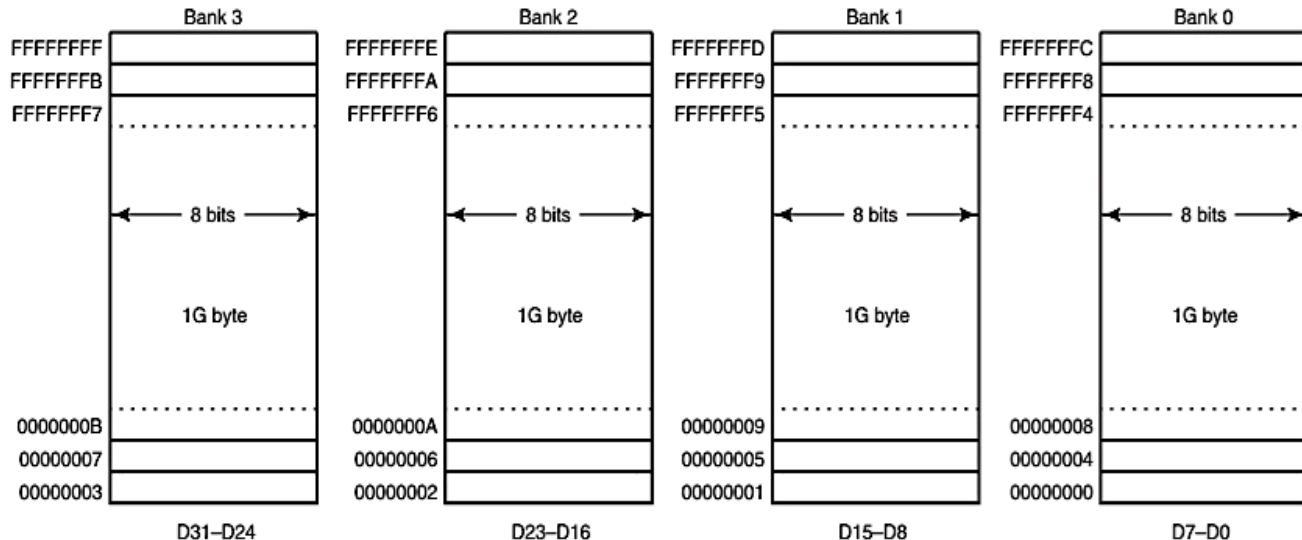


80386DX microprocessor  
80486SX microprocessor  
80486DX microprocessor






# Memory Address Decoding : NAND

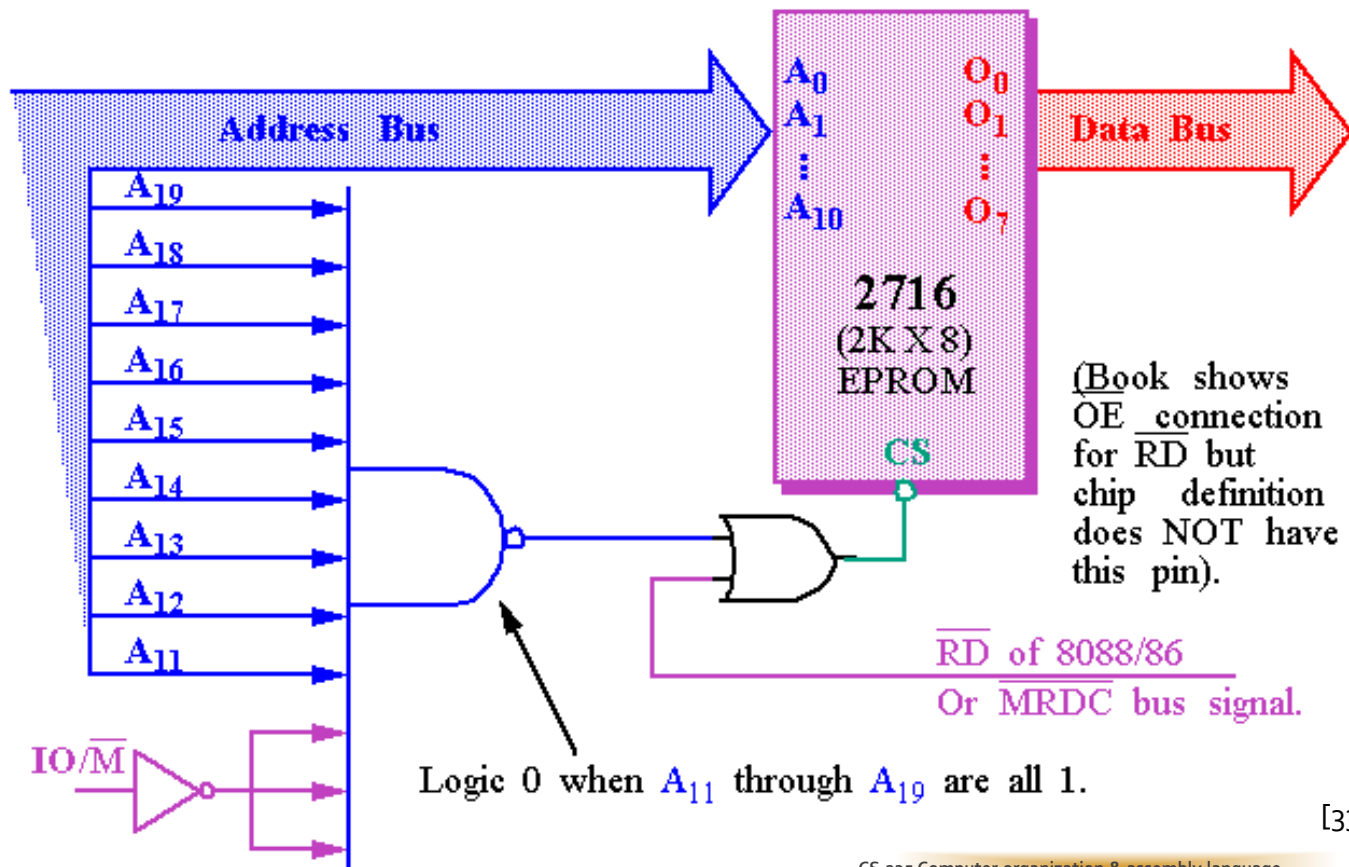




# Memory Address Decoding : 3 to 8

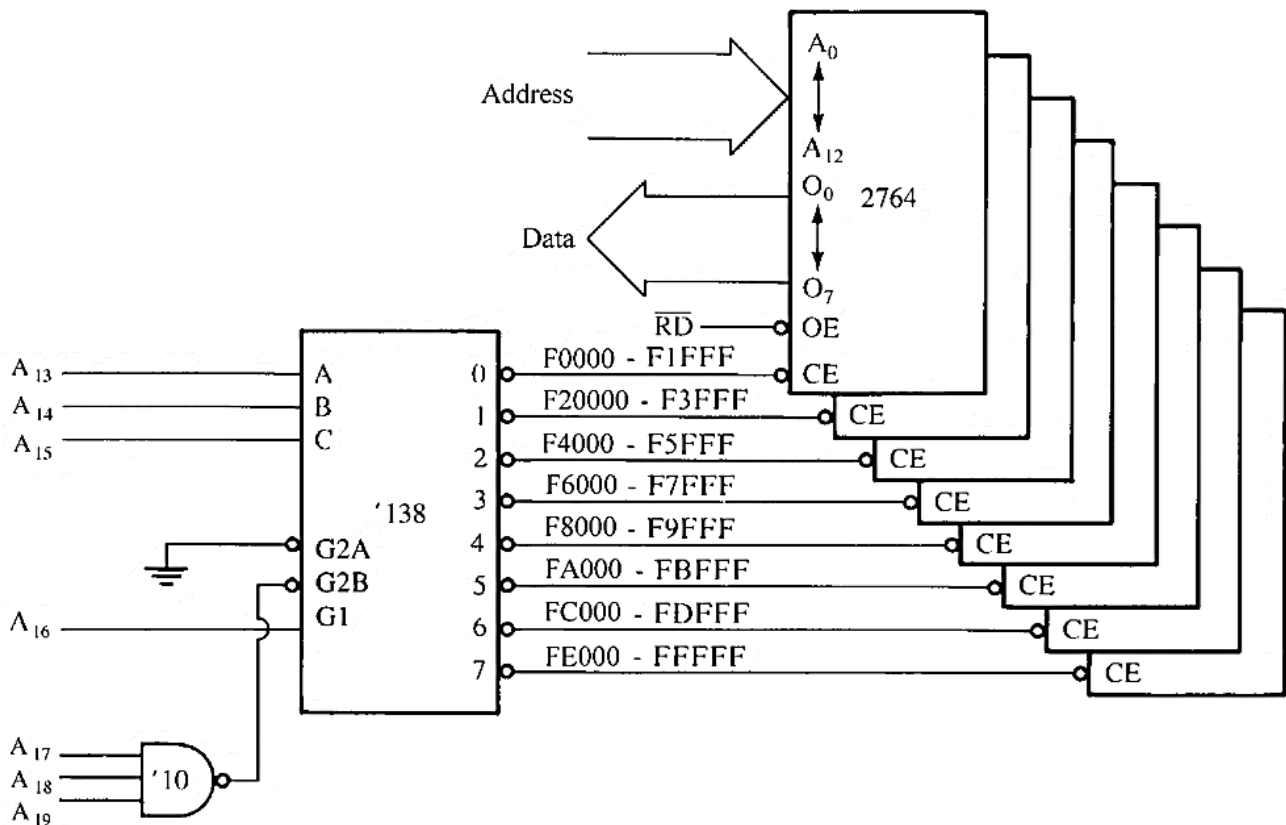




# Memory Address Decoding : 3 to 8

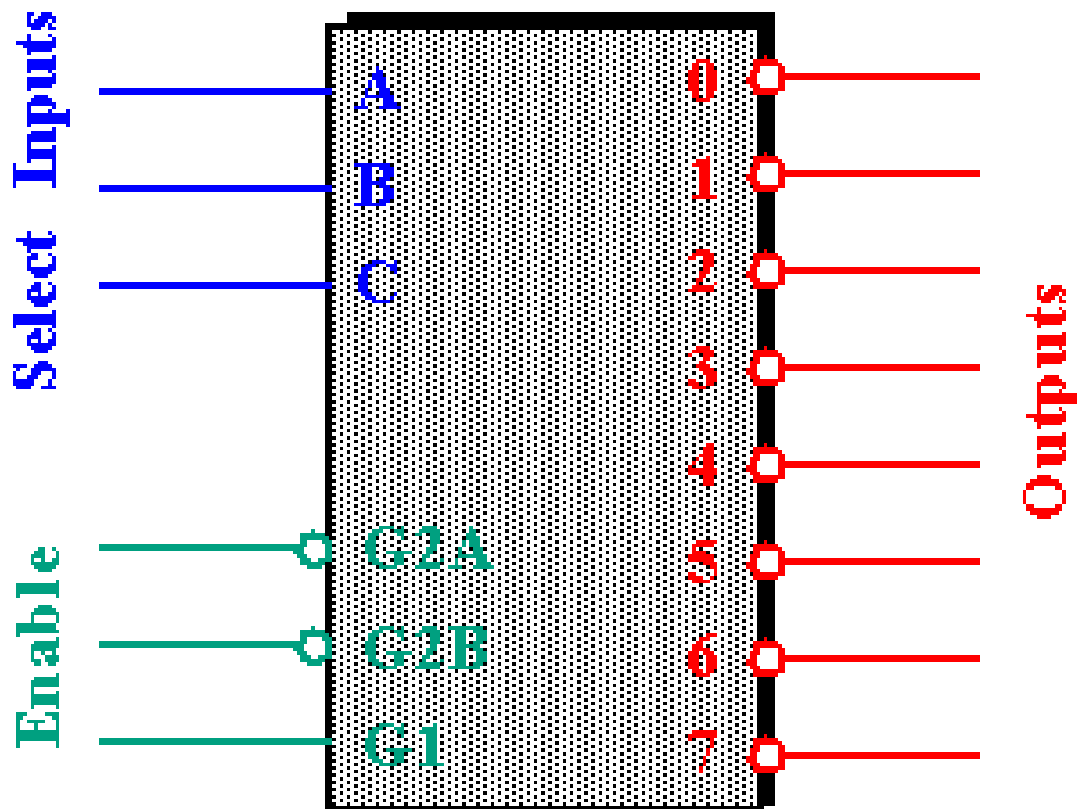



# Memory Address Decoding : 3 to 8

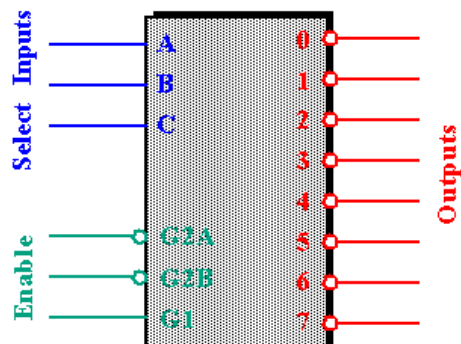

Inputs						Output							
Enable			Select										
G2A	G2B	G1	C	B	A	0	1	2	3	4	5	6	7
1	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	0	X	X	X	1	1	1	1	1	1	1	1
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	0	1	1	1
0	0	1	1	1	0	1	1	1	1	1	0	1	1
0	0	1	1	1	1	1	1	1	1	1	1	0	1


[36]


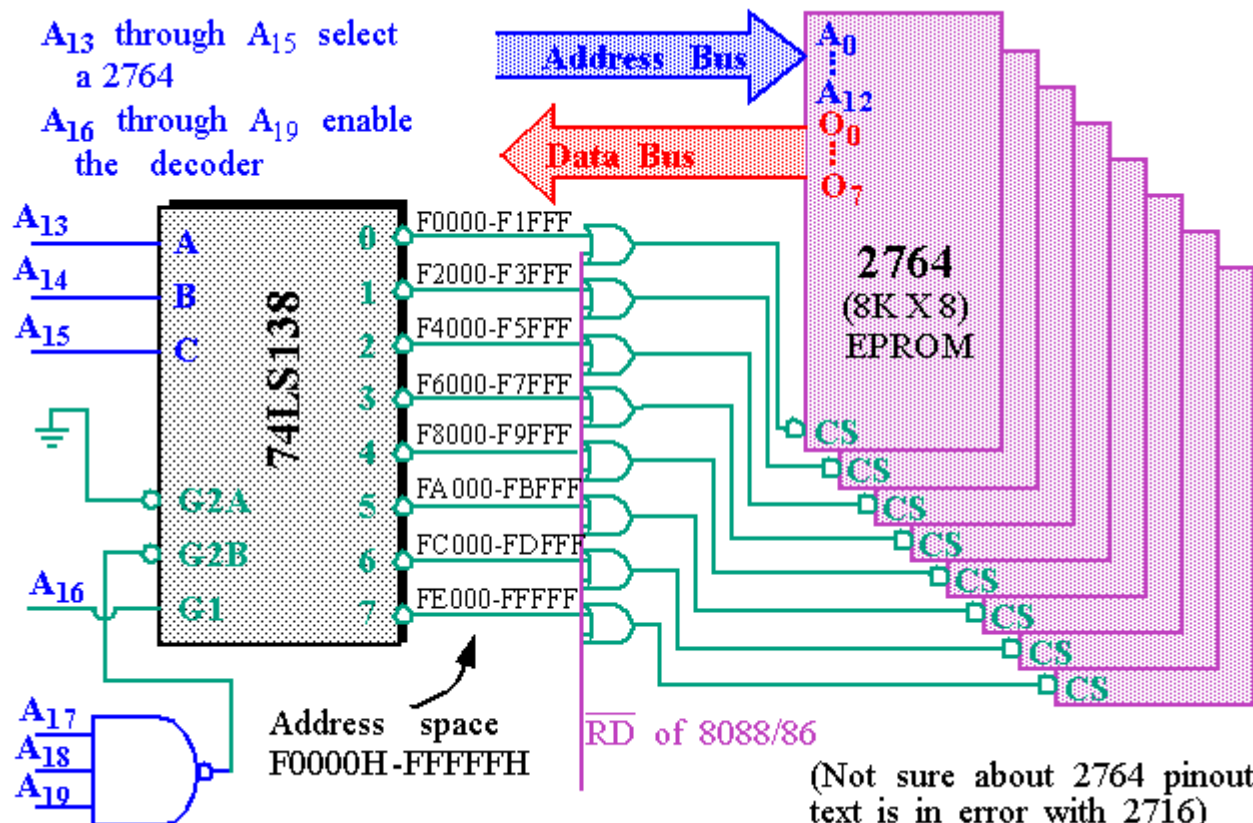
# Memory Address Decoding : 3 to 8

$A_{13}$  through  $A_{15}$  select  
a 2764

$A_{16}$  through  $A_{19}$  enable  
the decoder




(Not sure about 2764 pinout,  
text is in error with 2716)

[37]



# Memory Interfacing

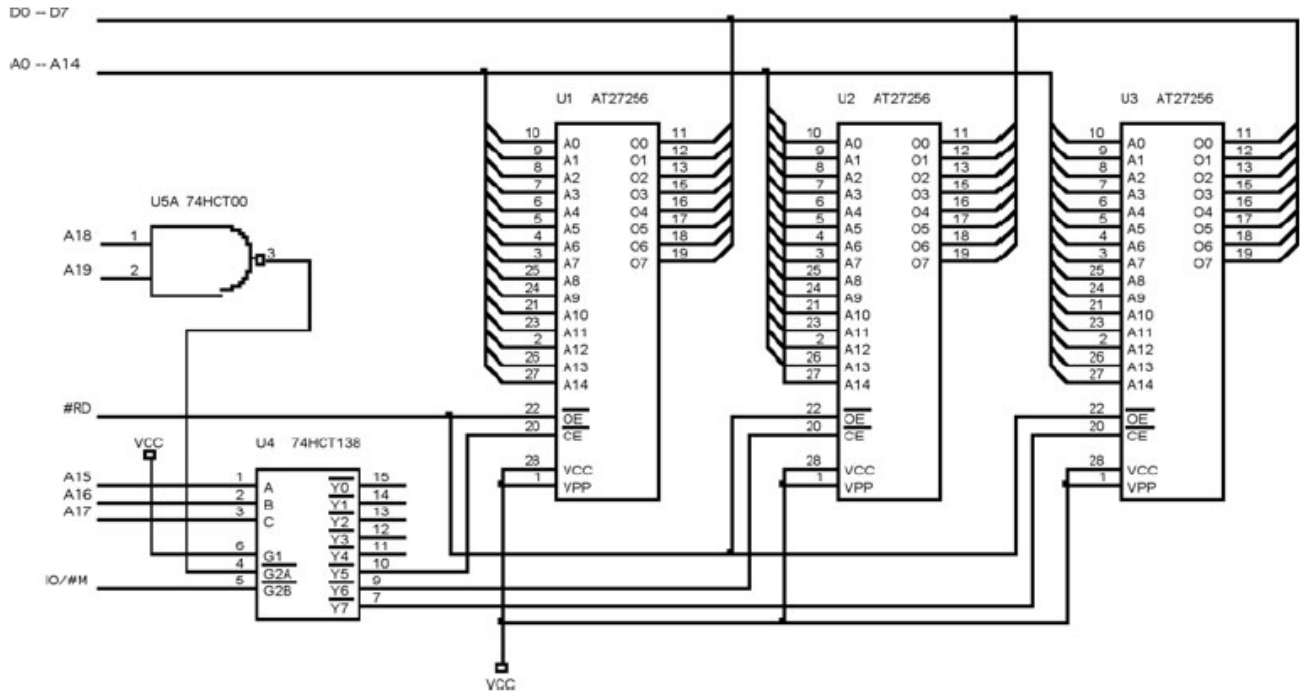

**FIGURE 10-20** Three 27256 EPROMs interfaced to the 8088 microprocessor.



## Method 3

### Programmable Logic Devices (PLDs)

These devices implement a Boolean function against each memory chip connection

- E-g. Programmable Logic Array (PLA)



# HM6264 & 27C256 RAM/ROM devices

- Low-cost low-capacity memory devices
- First two numeric digits indicate device type
  - RAM: 62
  - ROM: 27
- Subsequent digits
  - HM6264 → 8KB (13 address lines, 8 data lines)
  - 27C256 → 32KB (15 address lines, 8 data lines)



**Questions?**

**THANK YOU!**