 




Introduction to 8088/8086 Architecture



Topic 6
Fall 2019



Modes of operation

8086/8088 can be configured in **two modes**:

The minimum mode:

- Used for single processor system, where 8086/8088 directly generates all the necessary control signals

The maximum mode:

- Designed for multiprocessor systems, where an additional “**Bus Controller**” IC is required to generate the control signals. The processor controls the Bus controller using status codes



Pinout of 8086

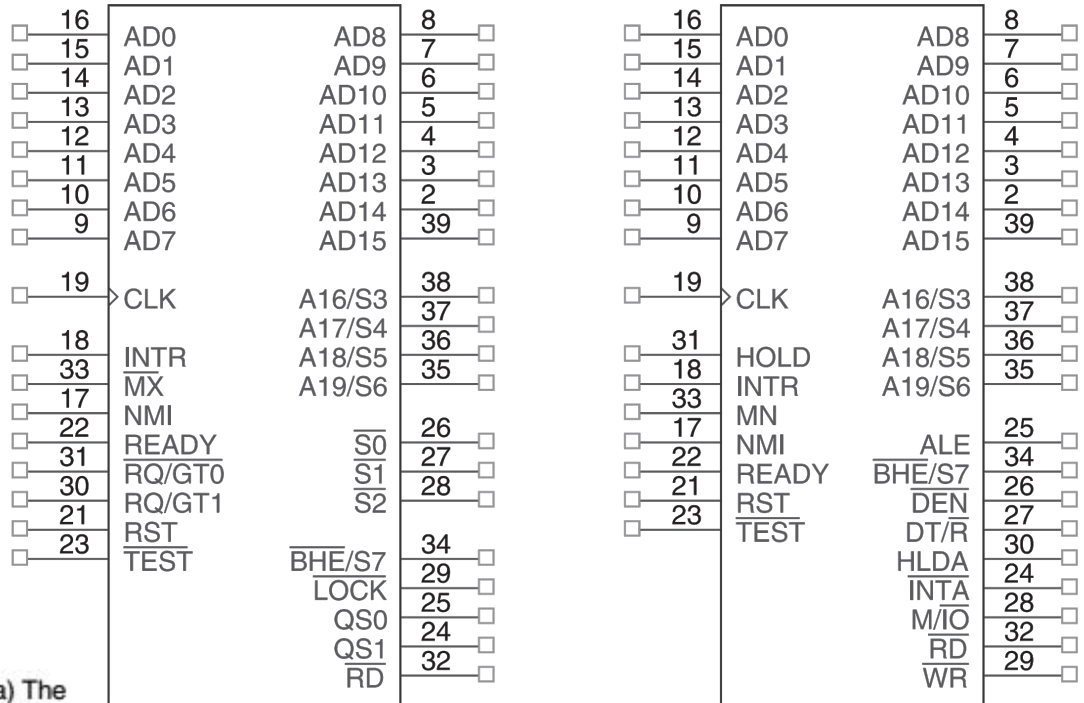


FIGURE 9-1 (a) The pin-out of the 8086 in maximum mode; (b) the pin-out of the 8086 in minimum mode.

8086MAX

(a)

8086MIN

(b)

[3]



Pinout of 8086

Clock (pin 19)

- 8284 clock generator IC is connected to 8086/8

Reset (pin 21)

- Reboots the microprocessor

Vcc (pin 40)


- Supply voltage

GND (Pin no. 1 & 20)

- Common Ground


MN/MAX (pin 33)

 - Select either minimum mode or maximum mode





Pinout of 8086

 

- 8088 operates at 5MHz to 8MHz
- 8086 operates at 5MHz to 10MHz



Fanout

- **Fanout:** Maximum number of digital inputs that a single logic gate can feed.
- Most TTL gates have **fan-out of 10**.
- In-order to extend number of connection beyond fan-out range, **buffers** are used.



[6]



Fanout of TTL standard

- A TTL signal must meet output & input voltage and current specifications.
- OH = Output High
- IL = Input Low
- Fanout = 10

Output characteristics		Input characteristics	
V_{OL}	0.4 V max	V_{IL}	0.8V max
V_{OH}	2.4 V min	V_{IH}	2.0 V min
I_{OL}	16 mA max	I_{IL}	1.6 mA max
I_{OH}	400 μ A max	I_{IH}	40 μ A max

DC Fan – out

$$= \min \left(\left[\frac{I_{out\ high}}{I_{in\ high}} \right], \left[\frac{I_{out\ low}}{I_{in\ low}} \right] \right)$$





Fanout of TTL standard

- A TTL signal must meet output & input voltage and current specifications.
- OH = Output High
- IL = Input Low
- Fanout = 10

Output characteristics		Input characteristics	
V_{OL}	0.4 V max	V_{IL}	0.8V max
V_{OH}	2.4 V min	V_{IH}	2.0 V min
I_{OL}	16 mA max	I_{IL}	1.6 mA max
I_{OH}	400 μ A max	I_{IH}	40 μ A max

DC Fan – out
  
$$= \min \left(\left[\frac{I_{out\ high}}{I_{in\ high}} \right], \left[\frac{I_{out\ low}}{I_{in\ low}} \right] \right)$$






Fanout of TTL standard

- A TTL signal must meet output & input voltage and current specifications.
- OH = Output High
- IL = Input Low
- Fanout = 10

Output characteristics		Input characteristics	
V_{OL}	0.4 V max	V_{IL}	0.8V max
V_{OH}	2.4 V min	V_{IH}	2.0 V min
I_{OL}	16 mA max	I_{IL}	1.6 mA max
I_{OH}	400 μ A max	I_{IH}	40 μ A max


DC Fan – out
 
$$= \min \left(\left[\frac{I_{out\ high}}{I_{in\ high}} \right], \left[\frac{I_{out\ low}}{I_{in\ low}} \right] \right)$$






Bus Buffering And Latching

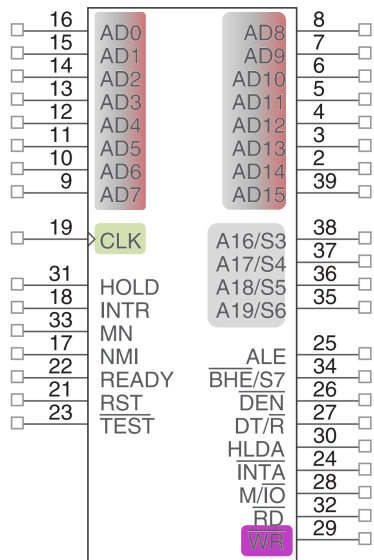


8086MIN

 




Bus Buffering And Latching

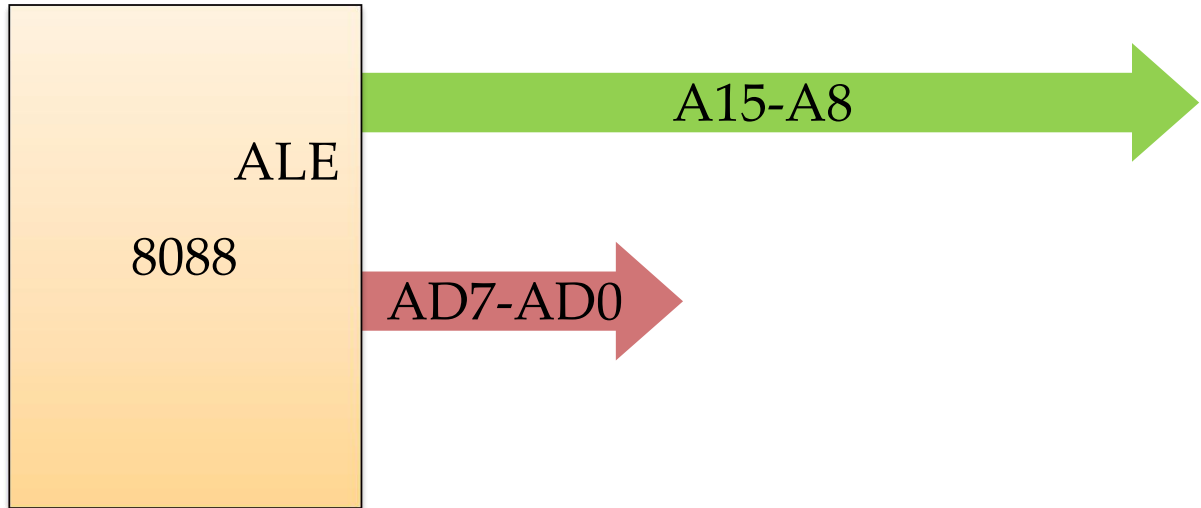



Bus Buffering And Latching

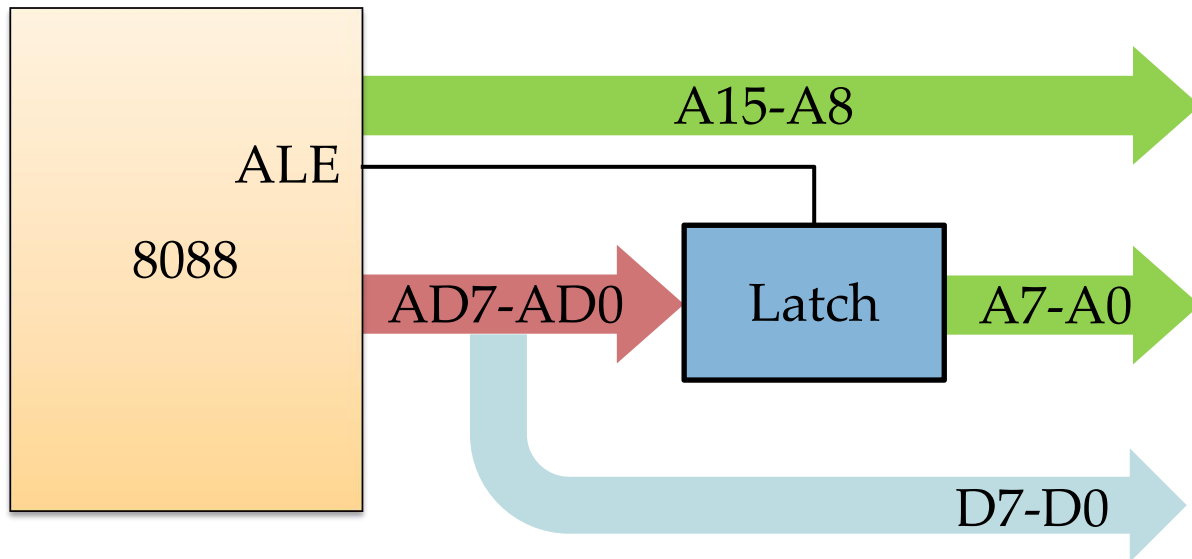



Bus Buffering And Latching

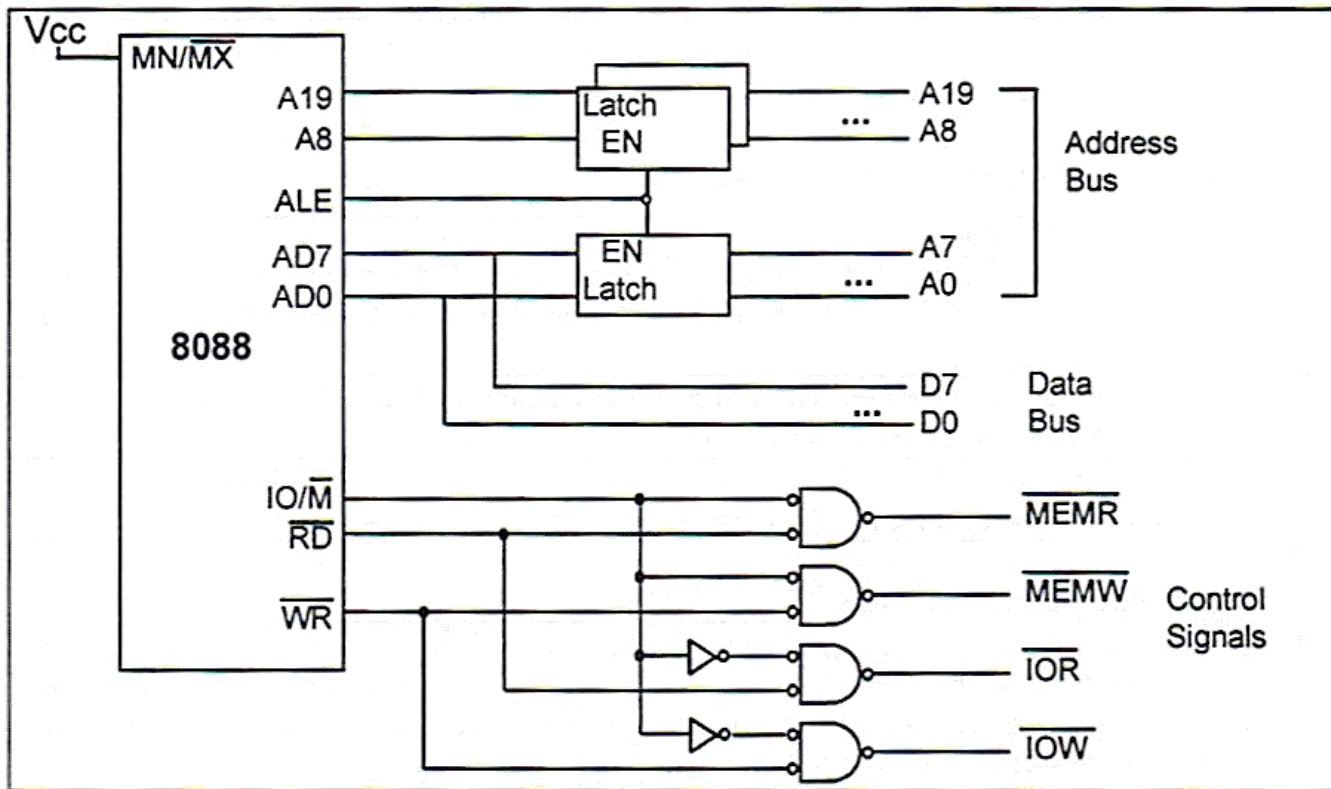


Figure 9-5. Address, Data, and Control Buses in 8088-based System



Bus Buffering And Latching

- Before the 8086/8088 microprocessors can be used with memory or I/O interfaces, their multiplexed buses must be demultiplexed.

 


FIGURE 9-5 The 8088 microprocessor shown with a demultiplexed address bus. This is the model used to build many 8088-based systems.



Bus Buffering And Latching

- Before the 8086/8088 microprocessors can be used with memory or I/O interfaces, their multiplexed buses must be demultiplexed.

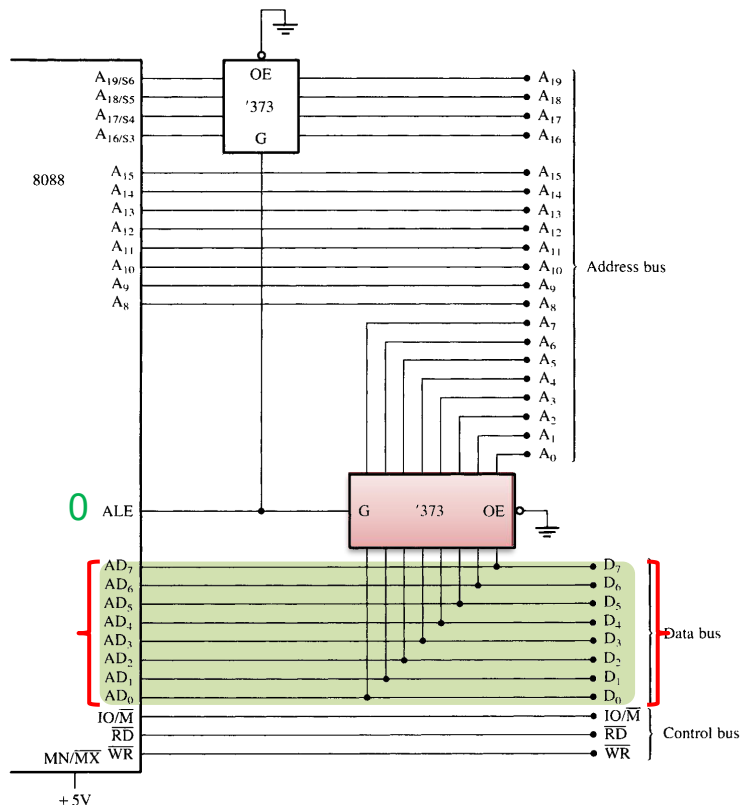



FIGURE 9-5 The 8088 microprocessor shown with a demultiplexed address bus. This is the model used to build many 8088-based systems.



Bus Buffering And Latching


Using the ALE signal to Demultiplex:

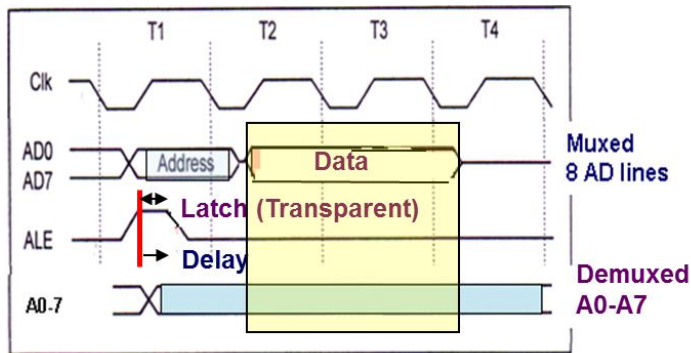- The Address lines A0-7 from the AD0-7 muxed bus
- The A16-19 lines from the A16/S3-A19/S6 muxed bus




Memory write cycle for the 8088
(non-muxed line are not shown)

 Data and address lines **must remain**
valid and stable for the duration of the cycle





De-multiplexing 8086 data/address bus

 



Non-DeMuxed Address Lines

→ 244 Buffer

DeMuxed Address Lines (unidirectional-Always O/Ps)


→ Latch provides the buffering

Non-Demuxed Bidirectional

Data Lines

→ 245 Buffer

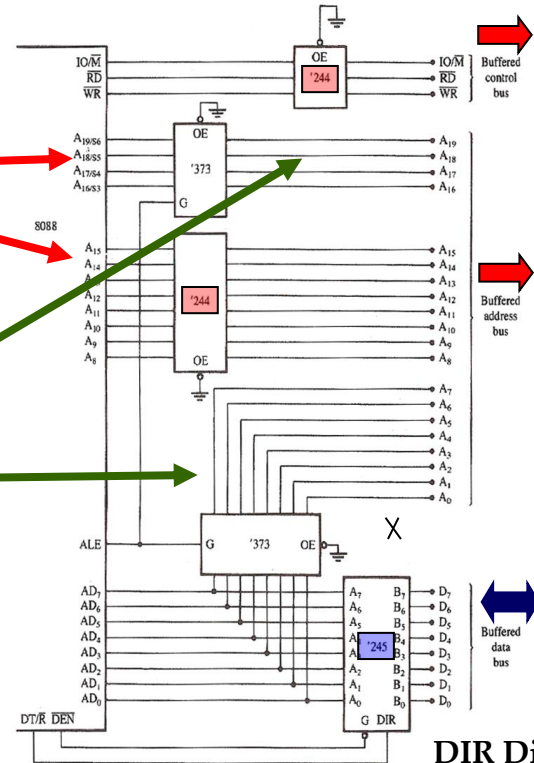74245 is an Octal Bus Transceiver
with 3-state outputs



Enable external buffers

DIR Direction


1: $A \rightarrow B$

0: $A \leftarrow B$

[18]



Fully DeMuxed & buffered 8086

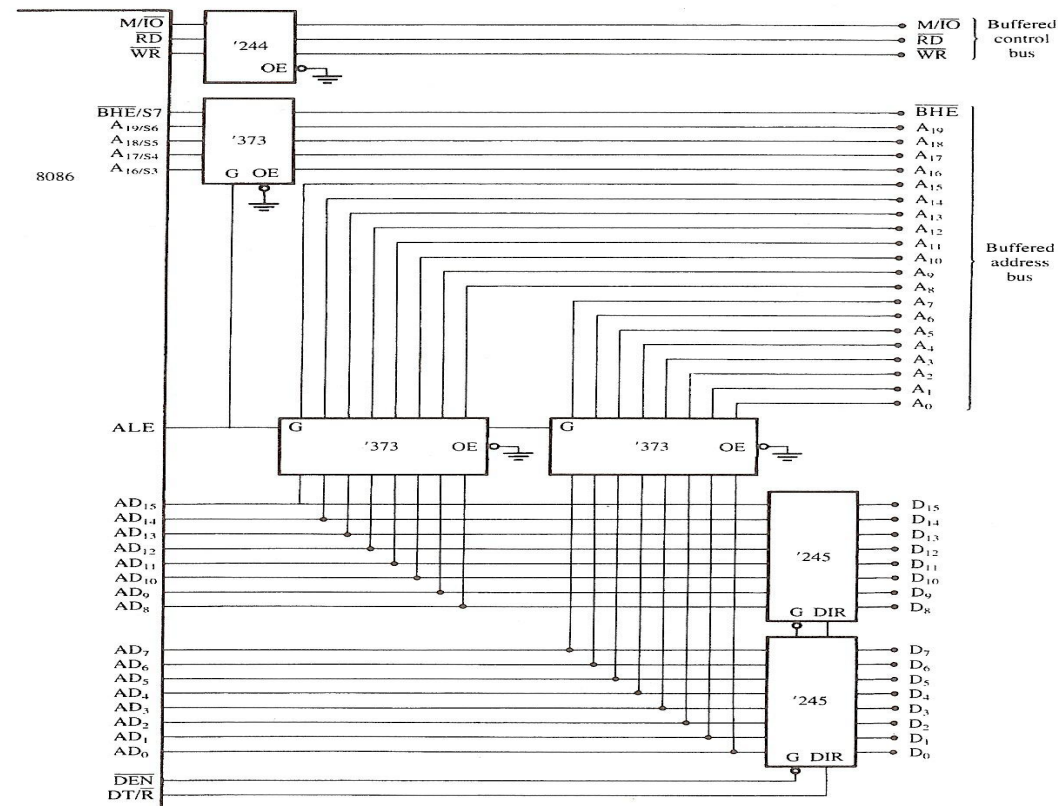



Book reference

- Intel microprocessor by Barry B. Brey.
- Chapter 9

Questions?

THANK YOU!